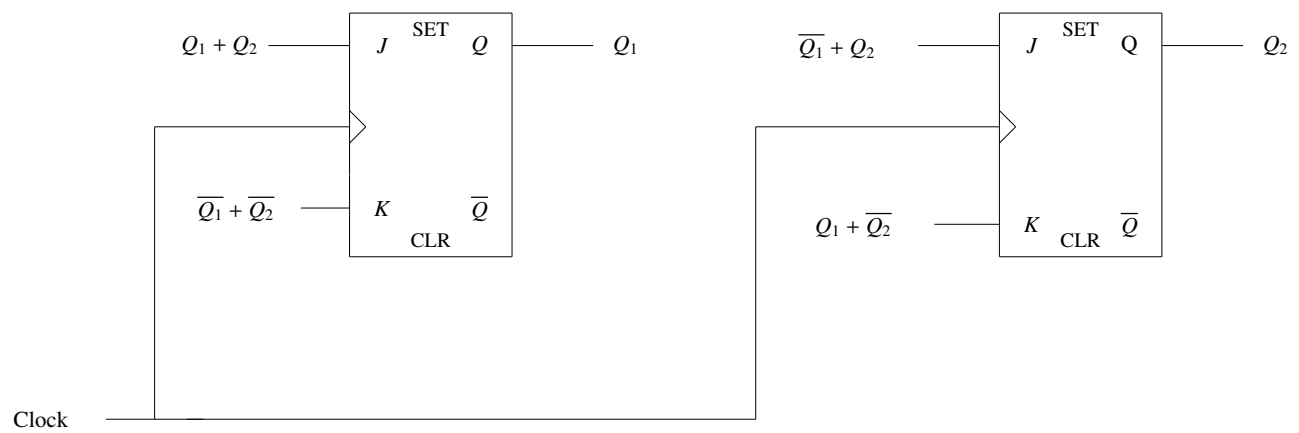


Gate IN2018, 44

Aryan Jain* FWC22256

February 19, 2024

A 2-bit synchronous counter using two J-K flip flops is shown. The expression for the inputs to the J-K flip flops are also shown in the figure. The output sequence of the counter starting from $Q_1Q_2 = 00$ is



- A. $00 \rightarrow 11 \rightarrow 10 \rightarrow 01 \rightarrow 00 \dots$
- B. $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \dots$
- C. $00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00 \dots$
- D. $00 \rightarrow 10 \rightarrow 11 \rightarrow 01 \rightarrow 00 \dots$